
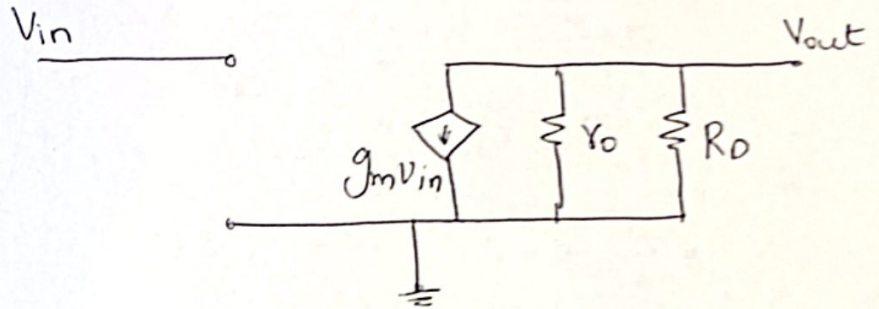


# Lec 18

(107)

## ● Single transistor amplifiers

### 1) Common Source (review)

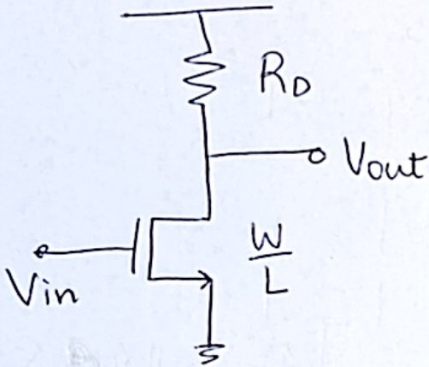

●  $\Rightarrow V_{out} = -g_m V_{in} (Y_0 \parallel R_D)$

$\Rightarrow A_v = -g_m (Y_0 \parallel R_D)$

### R<sub>in</sub>

Apply  $V_{test}$  & find  $i_{test}$ . In this case  $R_{in} = \infty$

### R<sub>out</sub>

●  $V_x = \frac{i_x \cancel{g_m V_{in}}}{Y_0 \parallel R_D} (i_x - \cancel{g_m V_{in}}) Y_0 \parallel R_D$



$\Rightarrow R_{out} = Y_0 \parallel R_D$

> We discussed source degeneration & also the diode connected load.

Diode connected load

$$\left( r_m \ll r_{mb} \ll r_o \right)$$


100      1k      10k

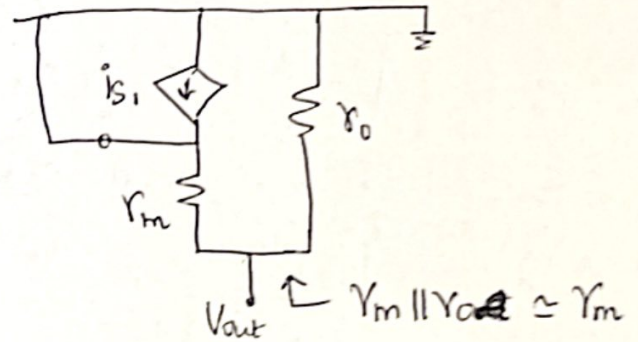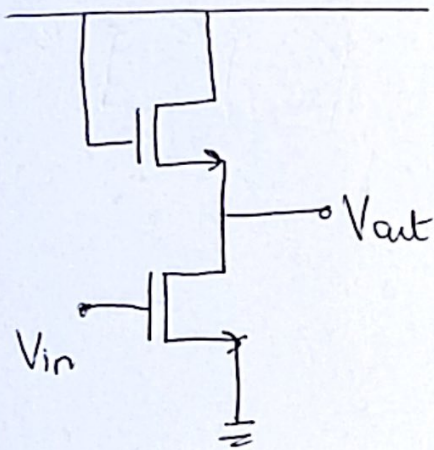

$$\Rightarrow A_v = -g_{m1} r_{m2}$$


$$= -\frac{g_{m1}}{g_{m2}} \approx -\sqrt{\frac{W_1/L_1}{W_2/L_2}}$$
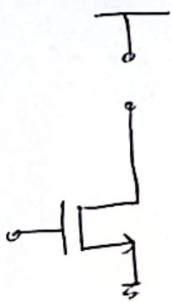
> Gain is low although it is well defined. What if I want to maximize the gain? We need an infinite resistor.




→ We need only an open in "small signal".

$$\frac{\partial I}{\partial V} = 0$$

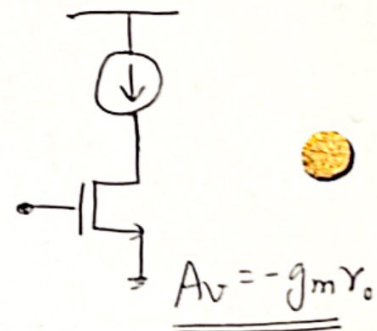


In practice we use a PMOS load.

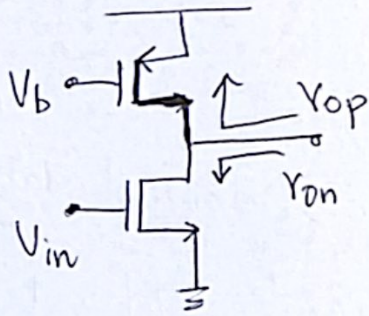

$$\Rightarrow A_v = -g_m (Y_{on} \parallel Y_{op})$$



### Common Drain (Source Follower)

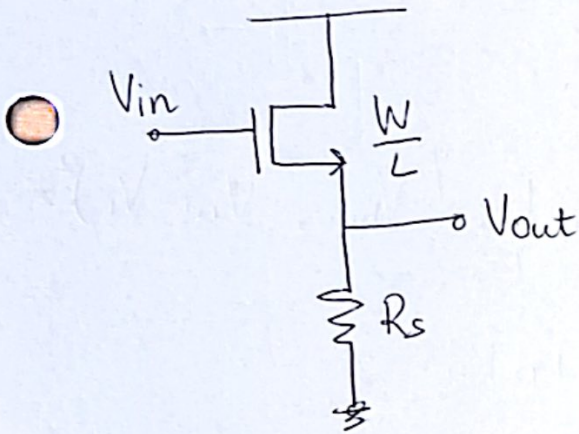

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_T)^2$$

$$V_{out} = R_s \left[ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_T)^2 \right]$$

### Small Signal Model

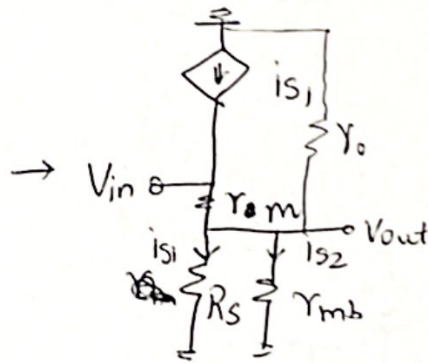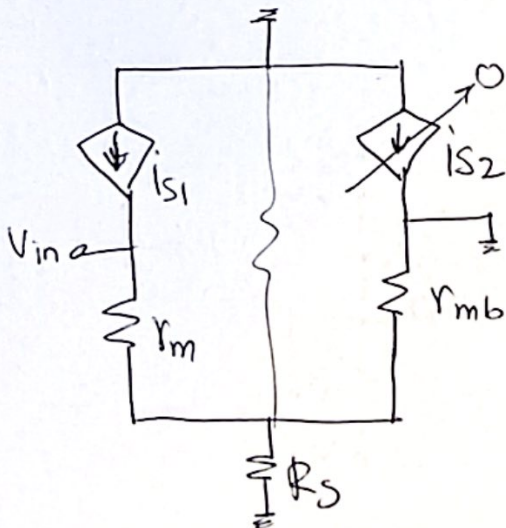

$$\Rightarrow A_v = \frac{R_s \parallel Y_{mb}}{R_s \parallel Y_{mb} + r_m} = \frac{R_s}{r_m + R_s(1 + \chi)}$$

$$\chi = \frac{g_{mb}}{g_m}$$

Note:  $A_v < 1$


Source Follower Since  $V_{out}$  closely follows  $V_{in}$  - Why is it useful?

$$R_{in} = \infty$$

$$R_{out} = R_s \parallel \gamma_m \parallel \gamma_{mb} < \gamma_m \rightarrow \text{good driver stage.}$$

Commonly used as a buffer stage.


## Common Gate

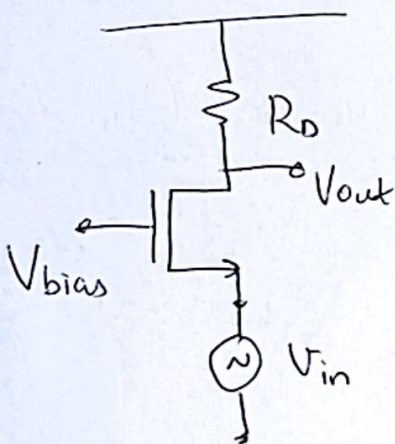


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{bias} - V_{in} - V_T)^2$$


$$V_{out} = V_{DD} - I_D R_o$$

## Small Signal Model

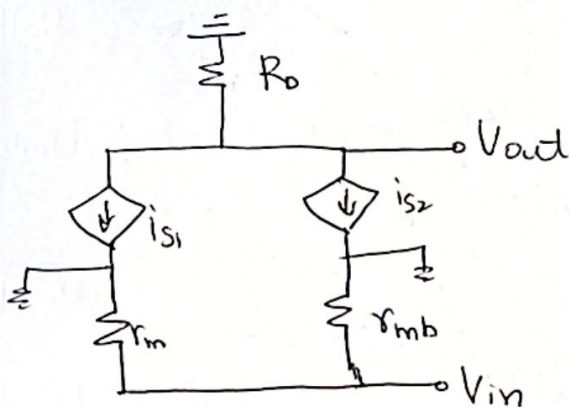

$\Rightarrow$

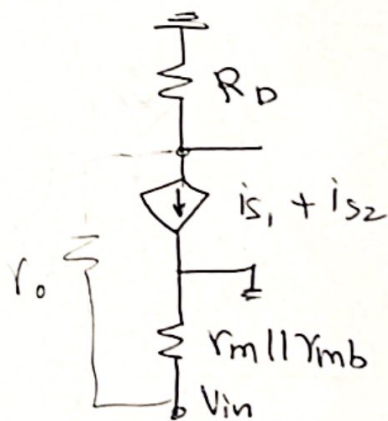

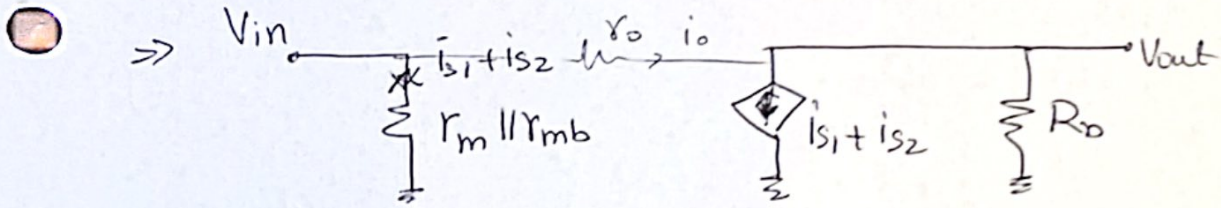

$$V_{out} = -(i_{s1} + i_{s2}) R_D = \left( V_{in} / (Y_m \parallel Y_{mb}) \right) R_D$$

$$\Rightarrow A_v = \frac{R_D}{Y_m \parallel Y_{mb}} = (g_m + g_{mb}) R_D$$

$$\Rightarrow \boxed{A_v = (g_m + g_{mb}) R_D} \rightarrow \text{Non inverting.}$$

Note: Here Body Effect increases the gain!

$$\left. \begin{array}{l} R_{in} = Y_m \parallel Y_{mb} \\ R_{out} = R_D \end{array} \right\} \text{Ignoring } r_o$$

Including  $r_o$

$$\$ V_{in} = \cancel{i_s (Y_m + Y_{mb})} + i_s (Y_m)$$

$$\frac{V_{in} - V_{out}}{r_o} = i_o$$

$$V_{out} = (i_o + i_s) R_D$$

$$V_{out} = \left[ \left( \frac{V_{in} - V_{out}}{r_o} \right) + \frac{V_{in}}{r_m} \right] R_p$$

$$V_{out} \left( \frac{1}{R_D} + \frac{1}{Y_o} \right) = V_{in} \left( \frac{1}{Y_o} + \frac{1}{r_m} \right)$$

$$\Rightarrow A_v = \frac{(R_D \parallel Y_o)}{(Y_o \parallel r_m)}$$

$$A_{vr} = \frac{R_D \parallel Y_o}{Y_o \parallel r_m \parallel Y_{mb}}$$

R<sub>out</sub>

$$R_{out} = R_D \parallel Y_o$$

$$R_{in} = Y_m \parallel Y_{mb} \parallel Y_o$$